




The University of Azad Jammu and Kashmir, Muzaffarabad

NAME	Jawahir Ali
ROLL NO	2024-SE-34
COURSE TITLE	Computer Architecture and Logic Design
COURSE CODE	CS-1205
INSTRUCTOR	Madam Sidra
SESSION	2024-2028
LAB TITLE	Encoder & Decoder

Department of Software Engineering

Encoder: Encoder is a combinational circuit which is designed to perform the inverse operation of the decoder. An encoder has n number of input lines and m number of output lines. An encoder produces an m bit binary code corresponding to the digital input number. The encoder accepts an n input digital word and converts it into an m bit another digital word.

Block diagram

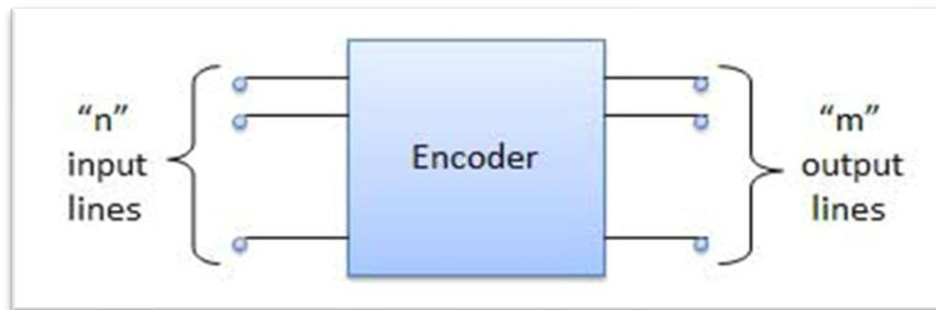

General Function:


- Number of input lines = 2^n
- Number of output lines = n

Example: 8-to-3 Encoder

Truth Table:

[illegible]

Circuit Diagram By (EWB)

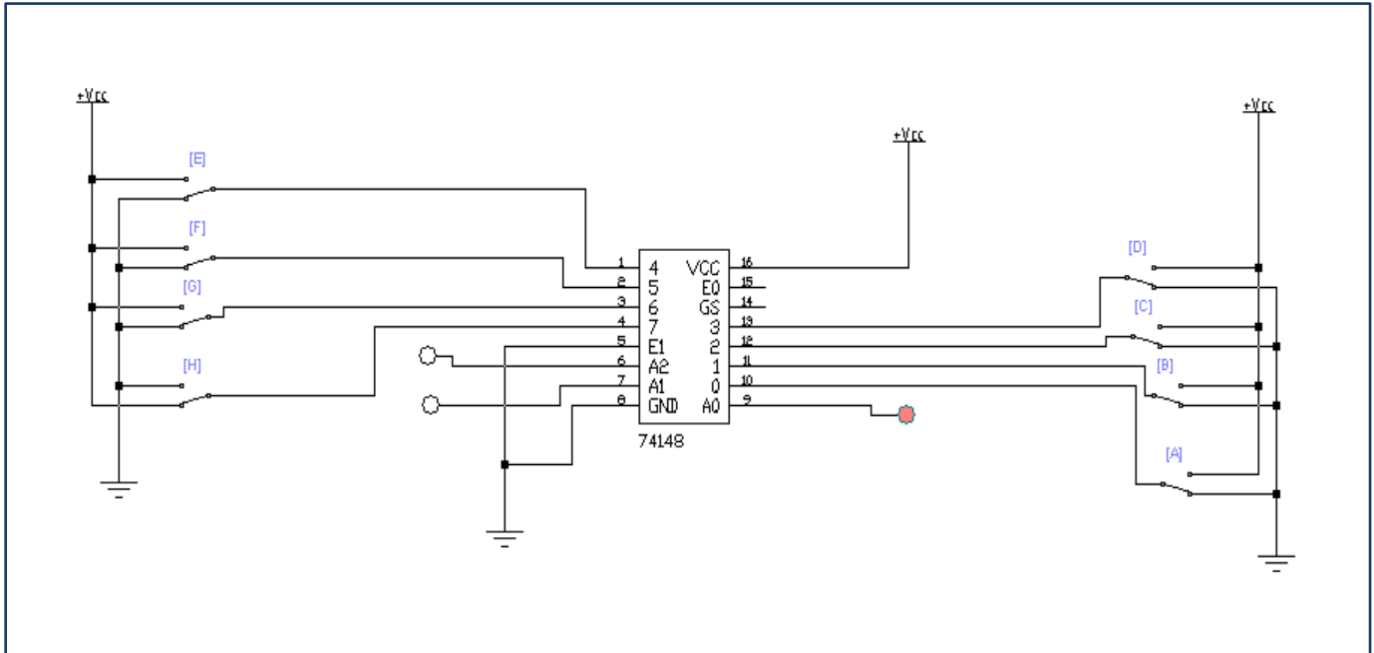

Output Expressions:

$$C = D4 + D5 + D6 + D7$$


$$B = D2 + D3 + D6 + D7$$

$$A = D1 + D3 + D5 + D7$$

Decoder: A decoder is a combinational circuit. It has n input and to a maximum $m = 2^n$ outputs.

Decoder is identical to a demultiplexer without any data input. It performs operations which are exactly opposite to those of an encoder.

Block diagram

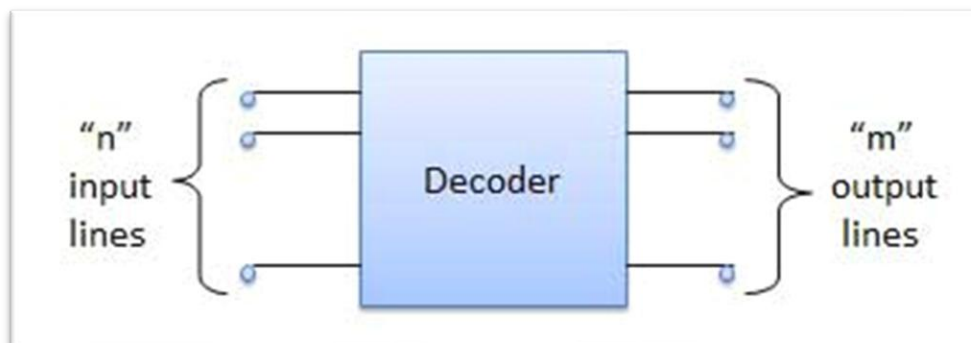

General Function:

- Number of input lines = **n**
- Number of output lines = **2ⁿ**

Example: 3-to-8 Decoder

Truth Table

C	B	A	Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Output Expressions:


$$Y_0 = EB'A'$$

$$Y_1 = EB'A$$

$$Y_2 = EBA'$$

$$Y_3 = EBA$$

Circuit Diagram By using (EWB)

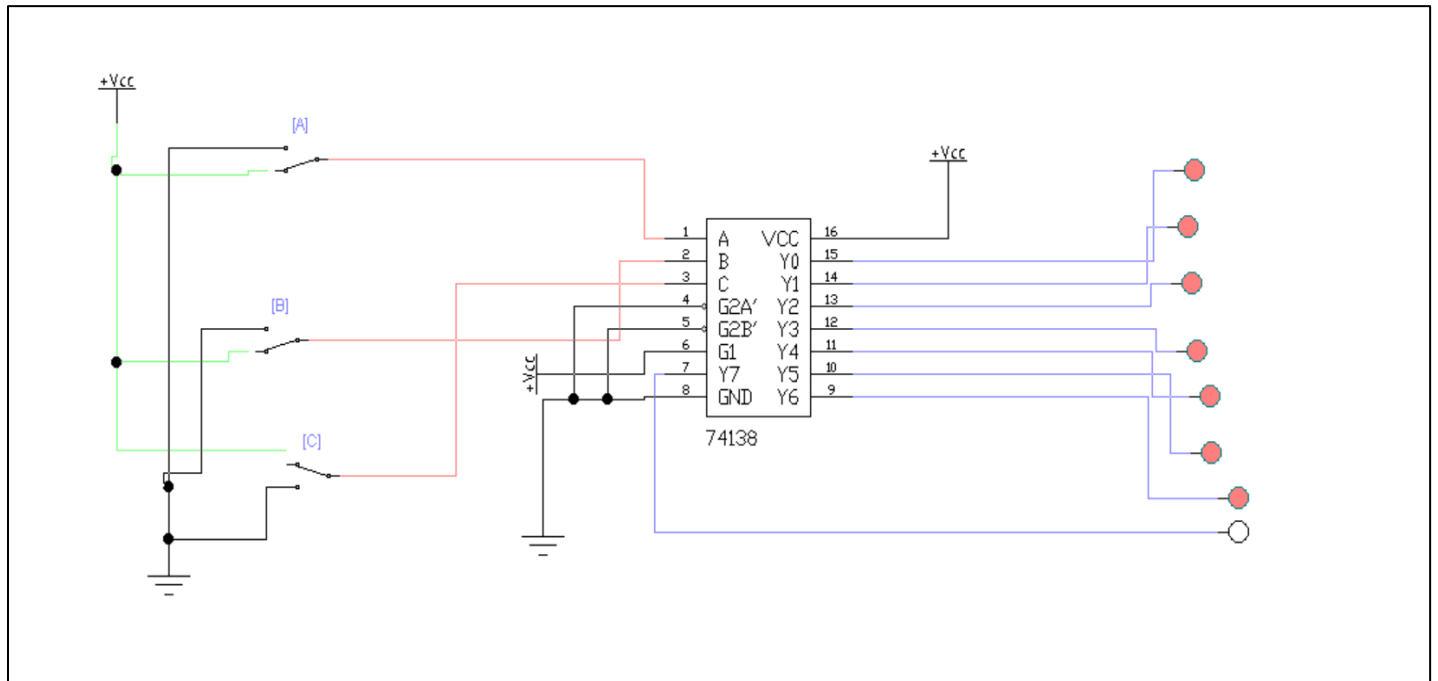

Best Of Luck